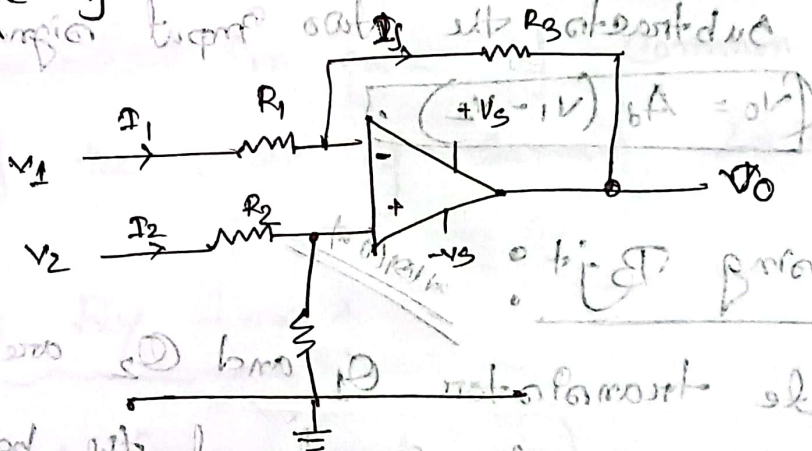


beg 7

Amplifier

Differential Amplifier

A device that is used to amplify the difference in voltage of the two input signals.



Subtractor
Differential
Amp

Characteristics: Def. Amp

- High voltage gain
- Low common mode gain
- High input impedance
- Low output impedance
- Low current

Operation Amplifier (OP-AMP)

An OP-AMP is a integrated circuit that can be amplify weak electric signals. It can perform some mathematical function like add, sub, differentiation and integration etc.

Differential Amplifier using op-AMP:

Because, of input configuration, all op-amp are considered to be differential amplifier.

- Differential amplifier behaves as subtractor circuit that basically subtracts the two input signals.

$$V_o = A_d (V_1 - V_2)$$

Voltage gain (Common mode gain)

$$A_c = \frac{V_o}{V_c}$$

output signal.
common input applied
to both input terminals.

CMRR (common mode rejection Ratio)

$$CMRR = \frac{A_d}{A_c}$$

ratio of diff. mode gain
to the common mode gain


• The larger the CMRR the better is the Amplifier

Logarithmic Amplifier

Log amp also called, It is an electronic device that produces output that is \propto of logarithm of the applied input.

- two circuits here $\left\{ \begin{array}{l} \text{Diode and op-amp} \\ \text{BJT and op-amp} \end{array} \right.$

A Log-Amp using diode and op-Amp:

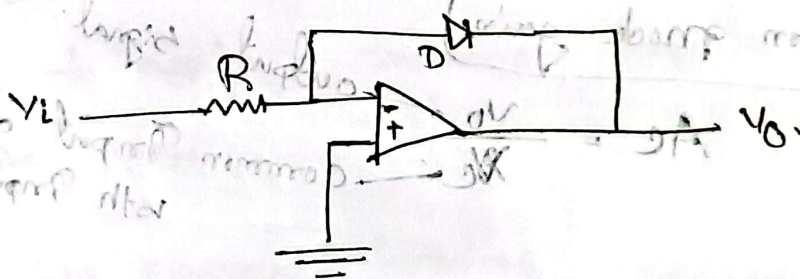


here op-Amp is ideal and negative feedback is present. voltage of inverting (V_-) and voltage of non inverting terminal (V_+) are ~~same~~ equal. according to virtual short concept

$$V_- = V_+ = 0V$$

Op-Amp ideal \therefore both terminals op-Amp, Zero.

Log amplifier using diode and op-Amp.

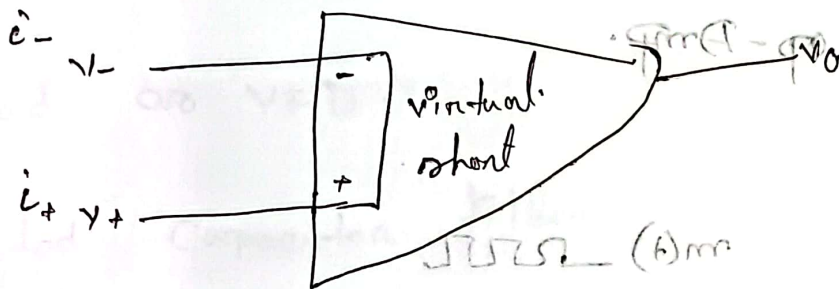Since, $V_- \approx V_+$ for feedback application, it appears that the 2 op-Amp terminals are connected together.




$$V_0 = -\eta \cdot V_T \ln \frac{V_i}{I_0 R}$$

180° phase difference.

Log amplifier using Diode and Transistor

voltage inverting terminal (V_-) is equal to voltage non-inverting terminal ($V_+ = 0V$) according to virtual short circuit.

$$V_- = V_+ = 0V$$

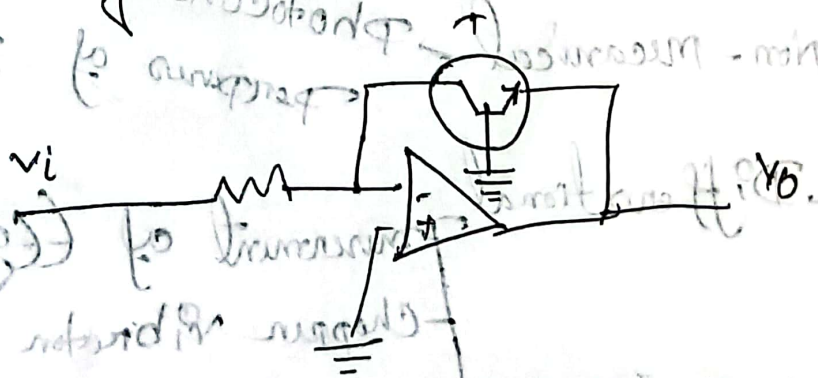

$$V_0 = -\eta V_T \ln \frac{V_i}{I_0 R}$$

emitter base junction

Display Device.

- Display Device are the output devices for presentation of information in image form.

Most commonly used display along with MC are LEDs, LCD, GLCD, and 7 segment displays.

Display using LED (Light emitting diode)

Used for indication of alarm, inputs and timers.

Two way

active high
Logic


It means
that LED
will on

When pin 1
when 0 off

Active Low
Logic

It means
LED will
off pin

90 0 1
on when
pin 0

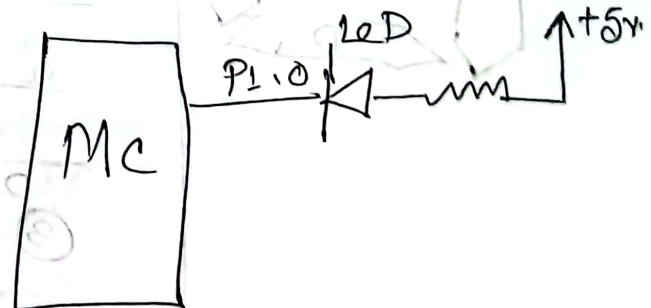




7 Segment LED Display.

It can be used for displaying digits and few characters.


• Display 0-9 digital ~~characters~~ information.

• Available for common anode and Cathode mode.
 Positive terminal Negative terminal


7 Segment LED

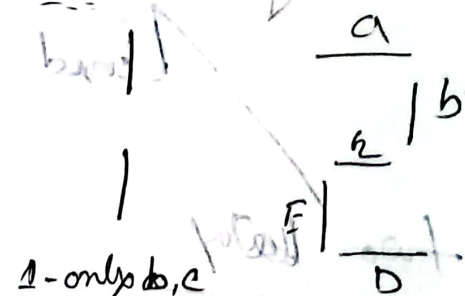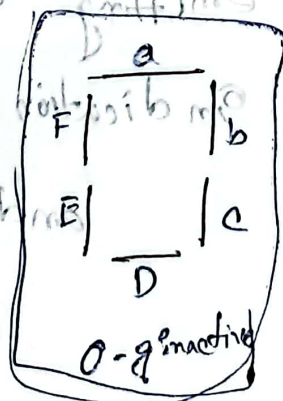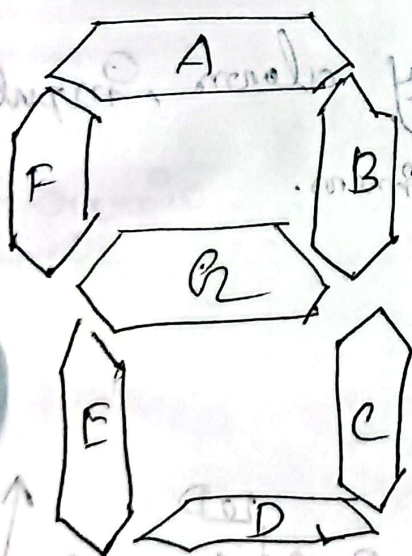


② F, C in active

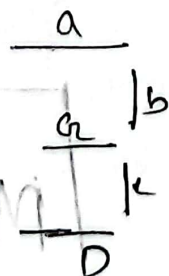

③

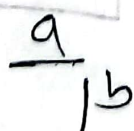


⑦

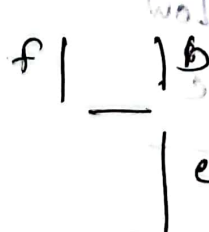


④



⑧

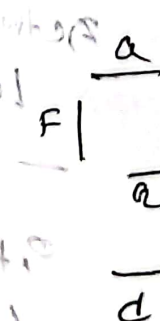

⑤

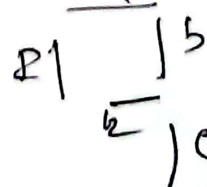


⑨


Dot matrix LED Display

It contains group of LEDs as a 2 dimensional array.

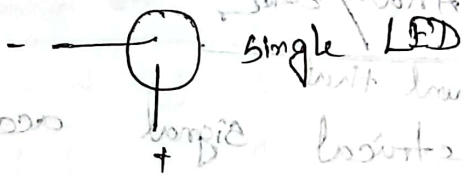
- It can display char and grp of char
- By using it we can reduce number of pin.
- Addressed by its row and column number



Dot Matrix

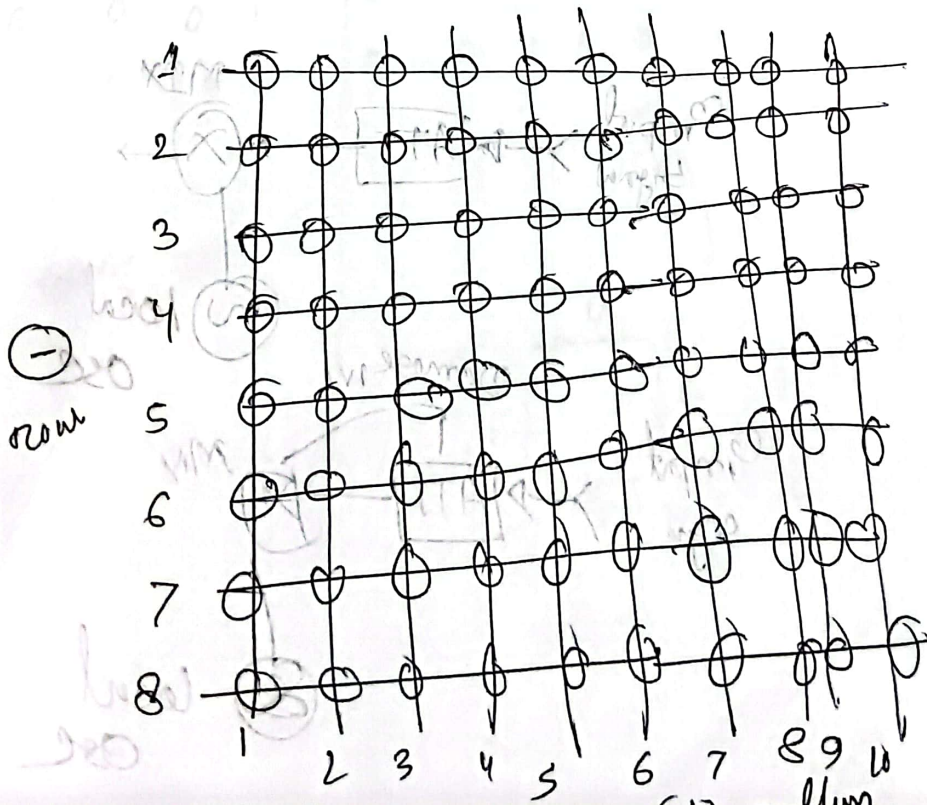

7 Seg Display

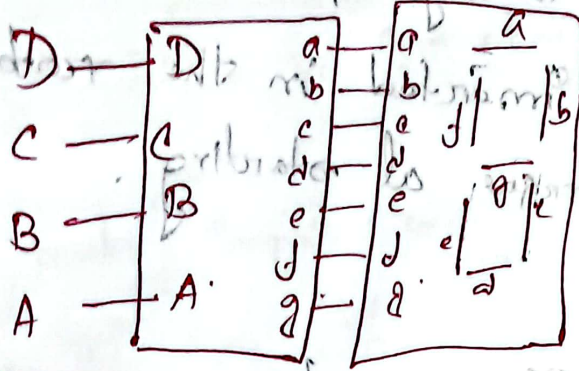

Truth table
mode: active low
Δ 0 1 2 3 4 5 6 7 8 9

Truth table Cathode Common

Num	A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	1
2	0	0	1	1	1	1	0	1	0	0	1
3	0	0	1	0	0	1	1	1	0	1	0
4	0	1	0	0	1	0	1	1	0	1	1
5	0	1	0	1	1	0	1	1	1	1	1
6	0	1	1	0	1	0	1	0	0	0	0
7	0	1	1	1	1	1	1	1	1	1	1
8	1	0	0	0	1	1	1	1	0	1	1
9	1	0	0	1	1	1	1	1	0	1	1