
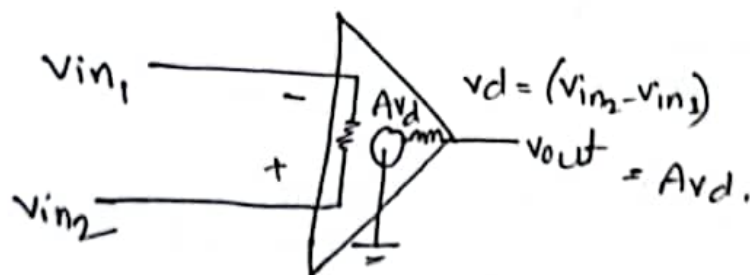


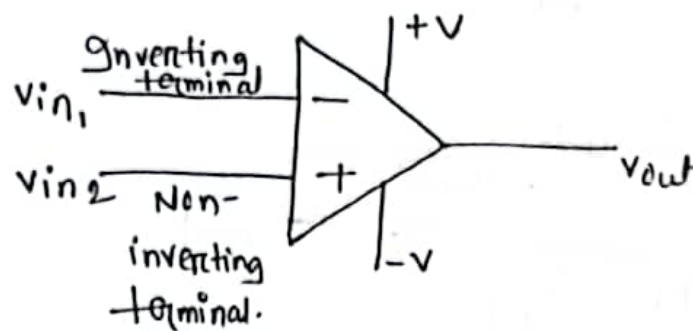
## Operational - Amplifier

OP-Amp: An operational Amplifier is an integrated circuit that can amplify weak electric signals & can perform some mathematical function like addition, Subtraction, Differentiation, Integration etc.

An OP-amp has high input impedance ( $\infty$ ) and low output impedance (0).



### Inverting Amplifier:-

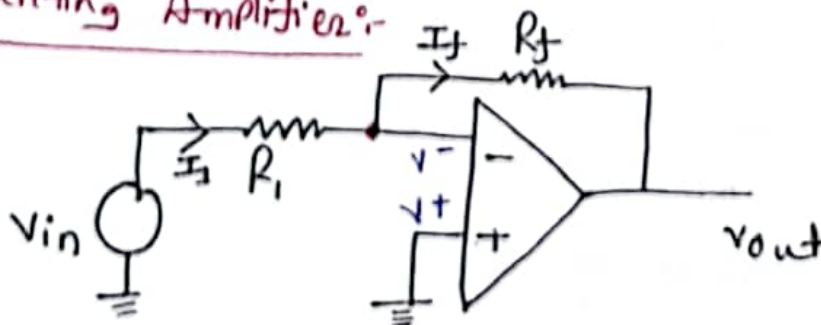

Apply KCL

$$I_1 - I_f = 0$$

$$I_1 = I_f$$

$$v^- = v^+ = 0$$

$$v^- = v^+$$


$$\therefore \frac{V_{in} - V^-}{R_1} = \frac{V^- - v_{out}}{R_f}$$

$$\frac{V_{in} - 0}{R_1} = \frac{0 - v_{out}}{R_f}$$

$$\frac{V_{in}}{R_1} = \frac{-v_{out}}{R_f}$$

$$\therefore \frac{v_{out}}{v_{in}} = -\frac{R_f}{R_1}$$

Non-inverting Amplifier:-

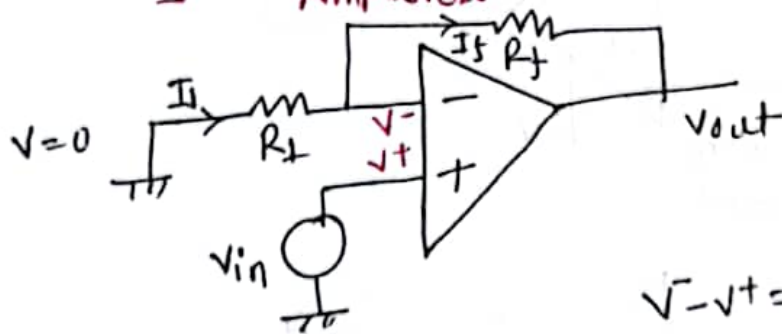

$$V^- - V^+ = 0$$

$$V^- = V^+$$

Here

$$\boxed{V_{in} = V^+ \therefore V^- = v_{in}}$$

$$I_1 = I_f$$

$$\frac{V^- - V_{in}}{R_1} = \frac{V_{in} - v_{out}}{R_f}$$

$$\frac{0 - v_{in}}{R_1} = \frac{v_{in} - v_{out}}{R_f}$$


$$-v_{in} R_f = v_{in} R_1 - R_1 v_{out}$$

$$-v_{in} R_f - v_{in} R_1 = -R_1 v_{out}$$

$$v_{in}(R_1 + R_f) = R_1 v_{out}$$

$$\frac{v_{out}}{v_{in}} = \frac{R_1 + R_f}{R_1} = \left(1 + \frac{R_f}{R_1}\right)$$

## Summing Amplifier:-

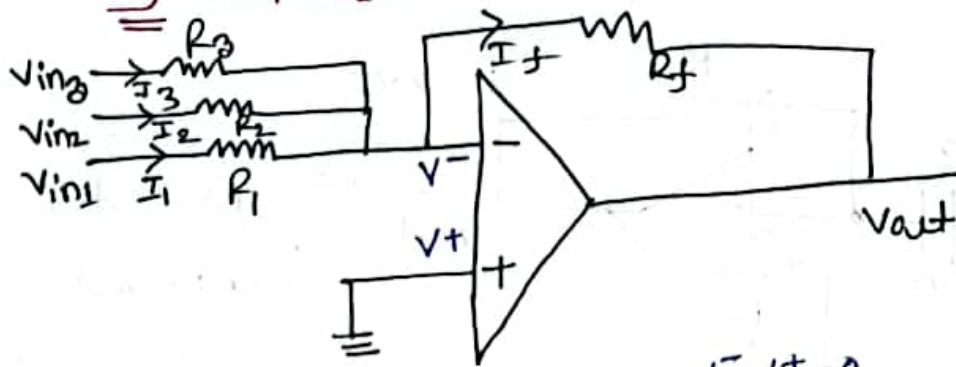

$$V^- = V^+ = 0$$

$$V^- = V^+$$

$$I_1 + I_2 + I_3 = I_f$$

$$\frac{V_{in1} - 0}{R_1} + \frac{V_{in2} - 0}{R_2} + \frac{V_{in3} - 0}{R_3} = \frac{0 - V_{out}}{R_f}$$


$$\frac{V_{in1}}{R_1} + \frac{V_{in2}}{R_2} + \frac{V_{in3}}{R_3} = \frac{-V_{out}}{R_f}$$

$$\therefore V_{out} = -R_f \left[ \frac{V_{in1}}{R_1} + \frac{V_{in2}}{R_2} + \frac{V_{in3}}{R_3} \right]$$

$$\text{if, } R_f = R_1 = R_2 = R_3 = R$$

$$\therefore V_{out} = -R \left[ \frac{V_{in1}}{R} + \frac{V_{in2}}{R} + \frac{V_{in3}}{R} \right]$$
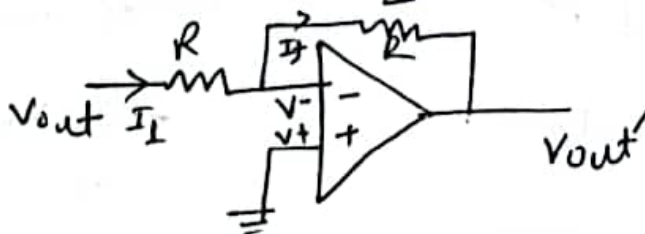
$$V_{out} = -[V_{in1} + V_{in2} + V_{in3}]$$




$$\frac{V_{out} - V}{R} = \frac{V - V_{out'}}{R}$$

$$V_{out} = -V_{out'}$$

$$\therefore V_{out'} = -V_{out}$$

$$= -[-(V_{in1} + V_{in2} + V_{in3})] = V_{in1} + V_{in2} + V_{in3}$$

## Differentiator:

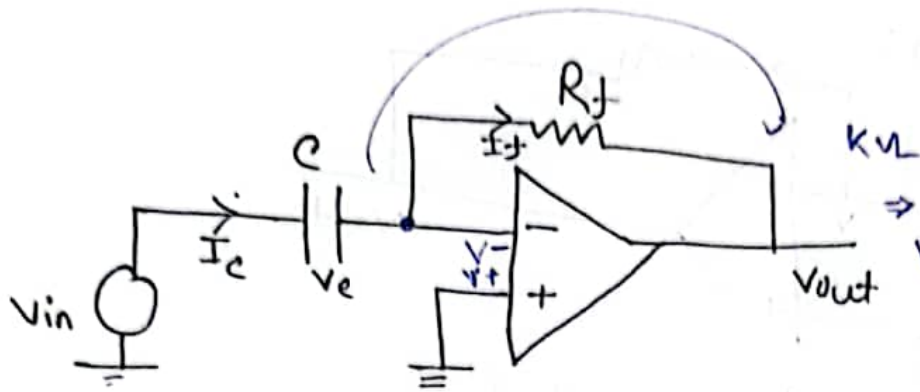

$$\begin{aligned} \text{KVL} \Rightarrow V^- - I_f R_f - V_{out} &= 0 \\ -I_f R_f &= V_{out} \\ \therefore V_{out} &= -I_f R_f \end{aligned}$$

$$I_c = I_f$$

the current eq<sup>n</sup> for Capacitor is

$$C \frac{dV_{in}}{dt} = \frac{V^- - V_{out}}{R_f}$$

$$I_c = C \frac{dV_c}{dt}$$

$$C \frac{dV_{in}}{dt} = \frac{-V_{out}}{R_f}$$


Here,

$$V_{in} = V_c$$

$$\therefore I_c = \frac{C dV_{in}}{dt}$$

$$\therefore V_{out} = -R_f C \frac{dV_{in}}{dt}$$

## Integrator →

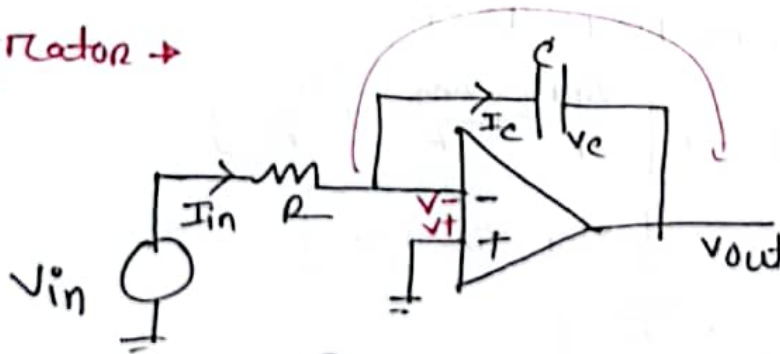

$$I_{in} = I_c$$

$$\frac{V_{in} - V^-}{R} = \frac{C dV_c}{dt}$$

$$\frac{V_{in}}{R} = C \frac{d}{dt} (-V_{out})$$

$$\frac{V_{in}}{R} = -C \frac{d}{dt} V_{out}$$

$$\text{KVL} \Rightarrow$$

$$V^- - V_c - V_{out} = 0$$

$$-V_c = V_{out}$$


$$\therefore V_c = -V_{out}$$

$$\frac{d}{dt} V_{out} = -\frac{V_{in}}{R_C}$$

Now, integrate on both side,

$$V_{out}(t) = -\frac{1}{R_C} \int V_{in}(t)$$

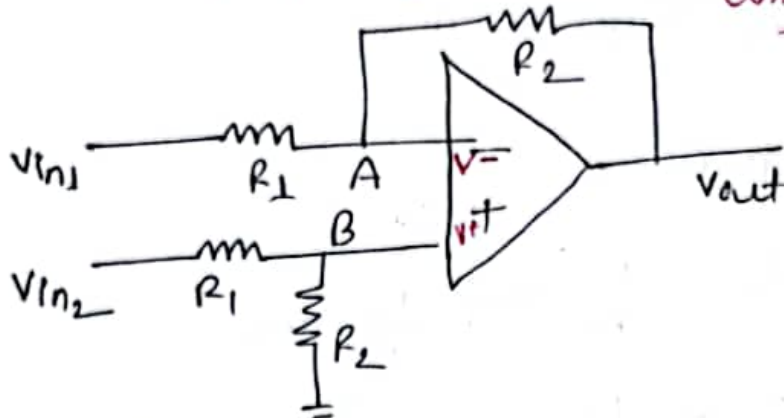Subtractor Amplifier  $\rightarrow$  (Differential Amplifier using OP-Amp)



Step-1: Select Inverting terminal

$$\frac{V_{in1} - V_A}{R_1} = \frac{V_A - V_{out}}{R_2}$$

$$V_- = V_+ = 0$$

$$V_- = V_+$$

Also,

$$V_- = V_A$$

$$\therefore \frac{V_{in1} - 0}{R_1} = \frac{0 - V_{out}}{R_2}$$

$$V_{out} = -\left(\frac{R_2}{R_1}\right) V_{in1} \quad \text{--- (1)}$$

Step-2: Select Non-Inverting terminal  $\rightarrow$

Apply Voltage Divider Rule in Point B

$$V_B = \frac{R_2 V_{in2}}{R_1 + R_2}$$

$$V.D.R \Rightarrow V_X = \frac{R_X E}{R_T}$$

Now, By using Non-inverting output eqn  $\rightarrow$

$$V_{out2} = \left(1 + \frac{R_2}{R_1}\right) V_B$$

$$= \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_2 V_{in2}}{R_1 + R_2}\right)$$

$$= \left(\frac{R_1 + R_2}{R_1}\right) \left(\frac{R_2 V_{in2}}{R_1 + R_2}\right)$$

$$V_{out2} = \frac{R_2}{R_1} V_{in2} \quad \text{--- (ii)}$$

$$\text{(ii)} - \text{(i)} \quad \text{or} \quad \text{(i)} - \text{(ii)}$$

$$V_{out1} - V_{out2} = \frac{R_2}{R_1} V_{in1} - \frac{R_2}{R_1} V_{in2}$$

$$V_{out} = \frac{R_2}{R_1} (V_{in1} - V_{in2})$$

$$\text{if } \Rightarrow R_2 = R_1 = R$$


$$\therefore V_{out} = \frac{R}{R} (V_{in1} - V_{in2})$$

$$V_{out} = V_{in1} - V_{in2}$$

~~the~~ Differential Amplifier/Op-Amp behave as a Subtractor Circuit.



Using op Amp and Transistor

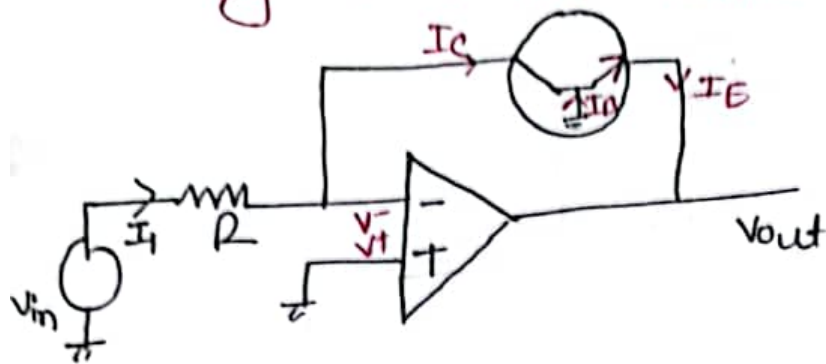

Here,

$$V_{BE} = V_B - V_E$$

$$I_E = I_B + I_C$$

$$I_B \approx 0$$

$$\therefore I_E = I_C$$

$$I_1 = I_C$$

$$\frac{V_{in} - V^-}{R} = I_C$$

the collector current eq<sup>n</sup>

$$I_C = I_S \left( e^{\frac{V_{BE}}{\eta V_T}} - 1 \right)$$

$$= I_S e^{\frac{V_{BE}}{\eta V_T}}$$

$$\therefore \frac{V_{in}}{R} = I_S e^{\frac{V_{BE}}{\eta V_T}}$$

$\eta$  = ideality factor

$I_S$  = Saturation current

$V_T$  = threshold voltage

$V_{BE}$  = Base-emitter voltage.

$I_C$  = Collector current.

Now,

$$V_{BE} = V_B - V_E$$

$$V_{BE} = 0 - V_E$$

$$V_E = -V_{BE}$$

↓


$$V_{out} = -V_{BE}$$

$$\therefore V_{BE} = -V_{out}$$

Now, we can write,

$$\frac{V_{in}}{R} = I_S e^{\frac{-V_{out}}{\eta V_T}} \quad [put, V_{BE} = -V_{out}]$$
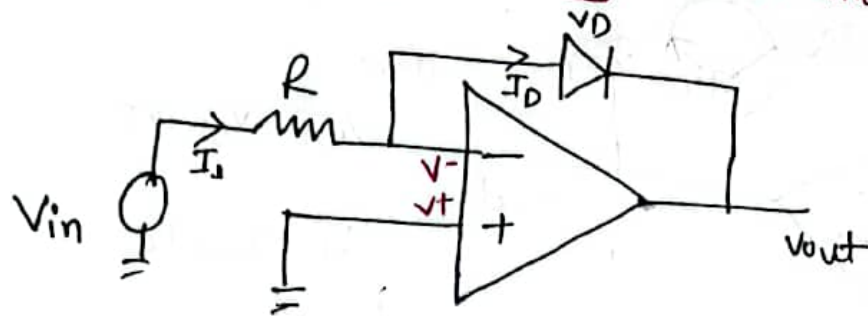
# Logarithmic Amplifiers using Diode and OP-Amp.



$$I_1 = I_D$$

$$\frac{V_{in} - V^-}{R} = I_0 e^{\frac{V_D}{\eta V_T}}$$

$$\frac{V_{in} - 0}{R} = I_0 e^{\frac{-V_{out}}{\eta V_T}}$$

$$\frac{V_{in}}{R} = I_0 e^{\frac{-V_{out}}{\eta V_T}}$$

$$e^{\frac{-V_{out}}{\eta V_T}} = \frac{V_{in}}{R I_0}$$

$$\ln e^{\frac{-V_{out}}{\eta V_T}} = \ln \frac{V_{in}}{R I_0}$$

$$\frac{-V_{out}}{\eta V_T} = \ln \frac{V_{in}}{R I_0}$$

$$V_{out} = -\eta V_T \ln \frac{V_{in}}{R I_0}$$

from diode  
current eq<sup>n</sup> →  
 $I_D = I_0 \left( e^{\frac{V_D}{\eta V_T}} - 1 \right)$

$$= I_0 e^{\frac{V_D}{\eta V_T}}$$

Here,

$\eta$  = ideality factor

$V_T$  = threshold voltage

$V_D$  = Diode voltage

$I_0$  or  $I_S$  = Saturation current

$I_D$  = diode current

$$V^- = V_D - V_{out} = 0$$

$$V_D = -V_{out}$$

\* Derive output voltage eq<sup>n</sup> for log Amplifier using Diode and OP-Amp.



$$e^{-\frac{V_{out}}{\eta V_T}} = \frac{V_{in}}{R I_S}$$

$$\ln e^{-\frac{V_{out}}{\eta V_T}} = \ln \frac{V_{in}}{R I_S}$$

$$\frac{-V_{out}}{\eta V_T} = \ln \frac{V_{in}}{R I_S}$$

$$-V_{out} = \eta V_T \ln \frac{V_{in}}{R I_S}$$

$$\therefore V_{out} = -\eta V_T \ln \frac{V_{in}}{R I_S}$$

\* Derive o/p voltage  $e_2^n$  for OP-Amp using transistor ... and OP-Amp.

OR OP-Amp can be used as a log Amplifier  $\rightarrow$  Prove.